


CMOS NAND GATE CHARACTERISTICS

Name: Bhavya Nagrath


Regn. No.: 21BEC0399

Lab Slot: L15+L16



1. NAND CMOS CIRCUIT

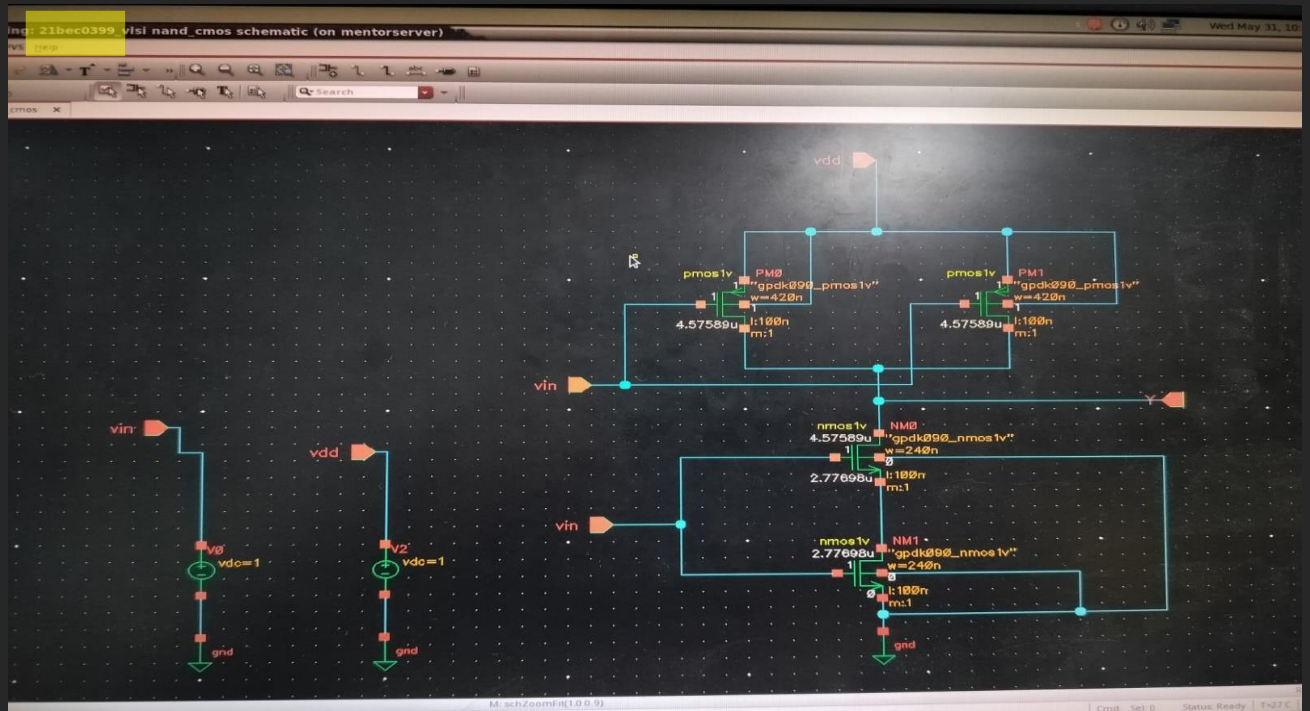



1. CASE 1: A=B= 0->1

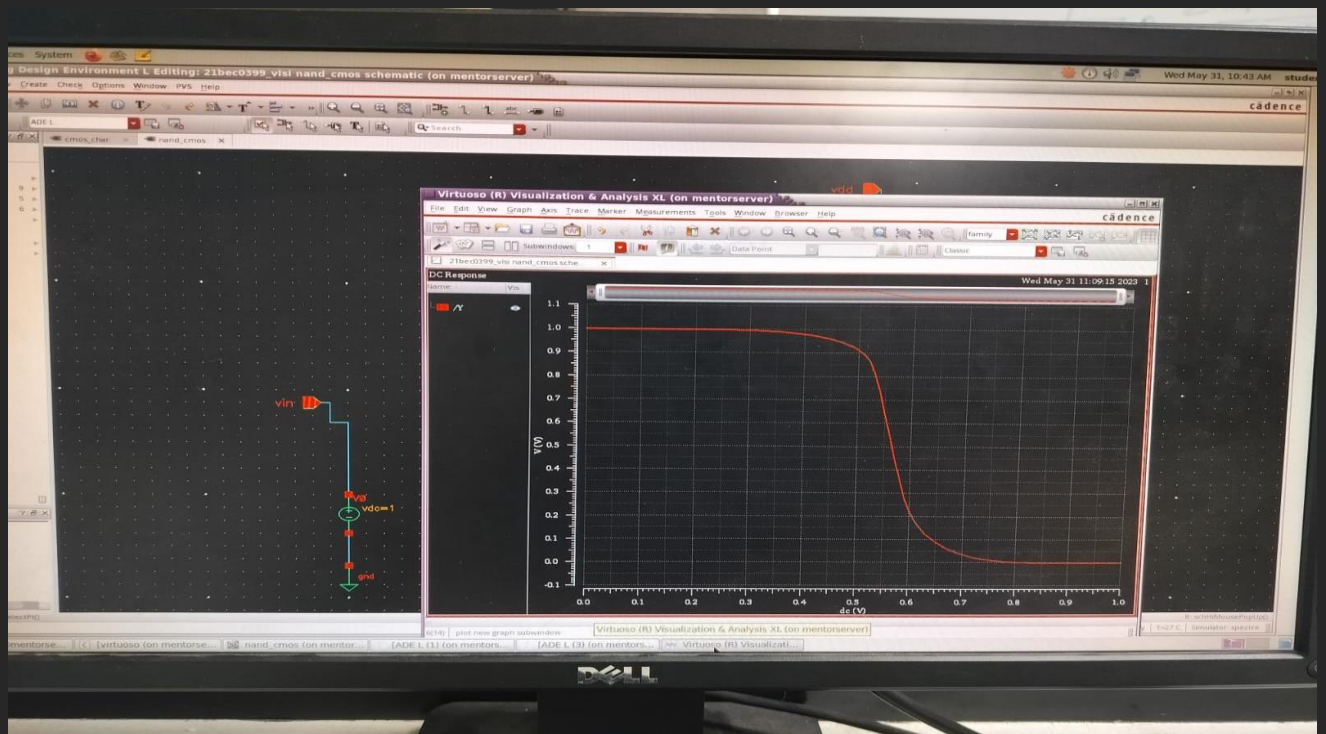



2. CASE 2 - When $A=1$ and B is on X-axis

 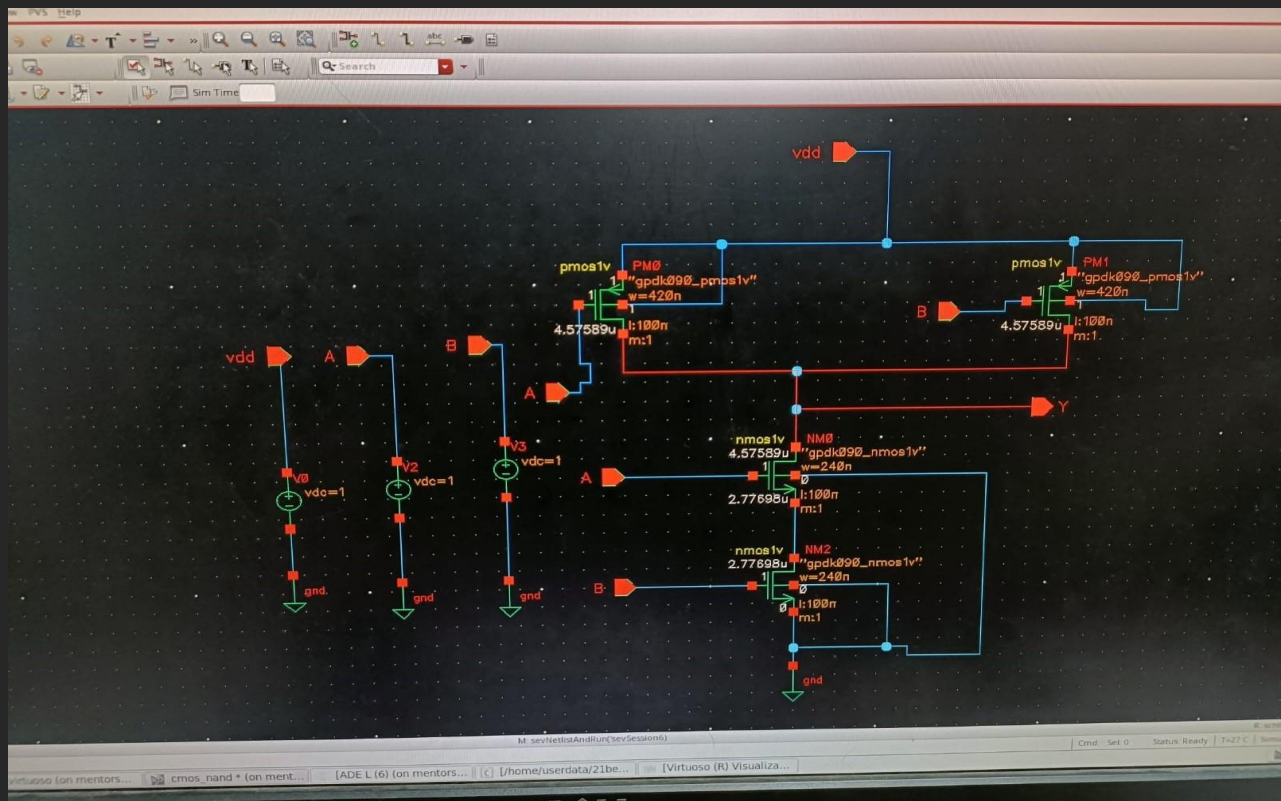



Case 3: When B=1 and A is on X-axis

 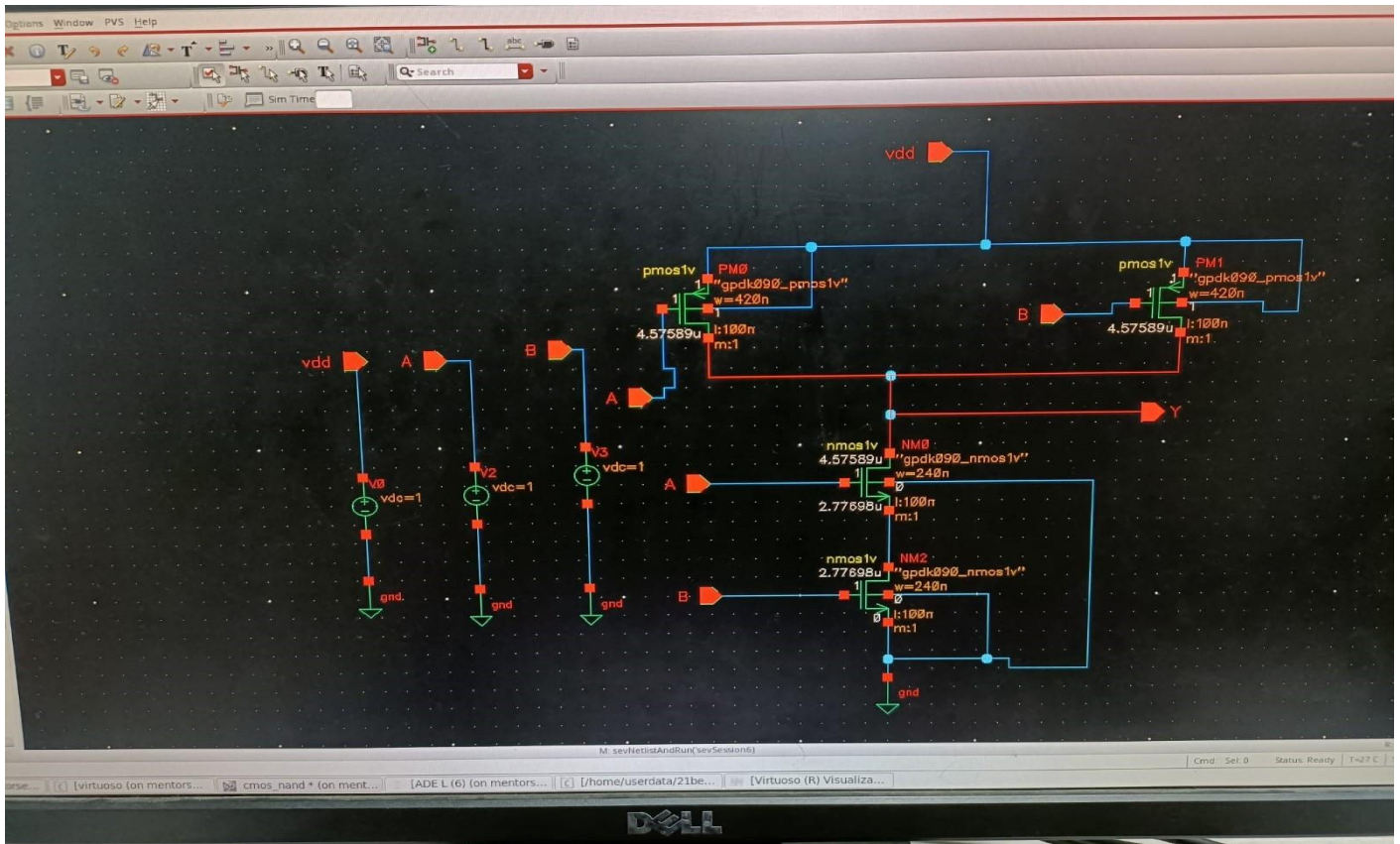



Case 4: When $A=0$ and B on X-axis

 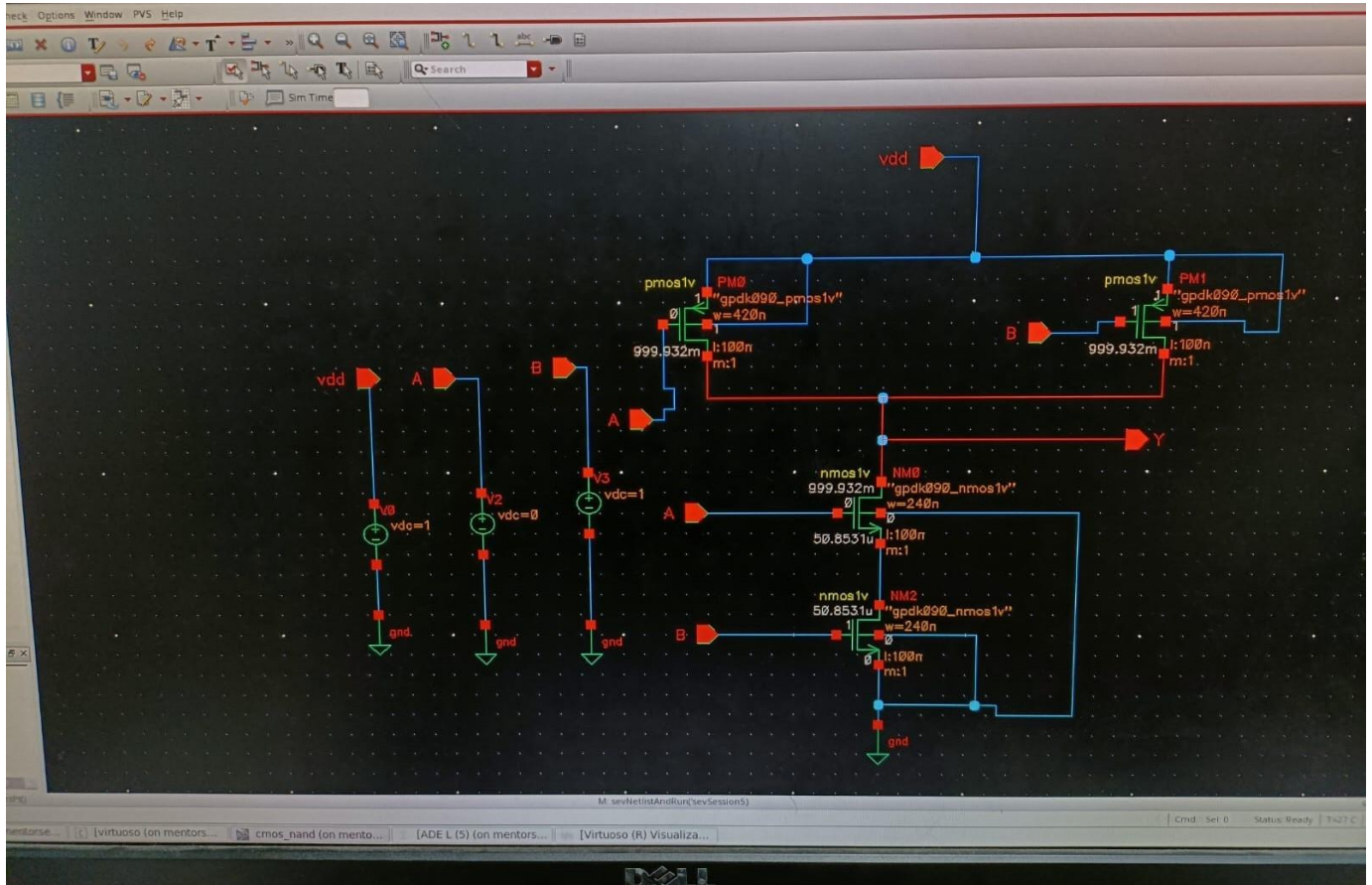

Case 5: When B=0 and A on X-axis

 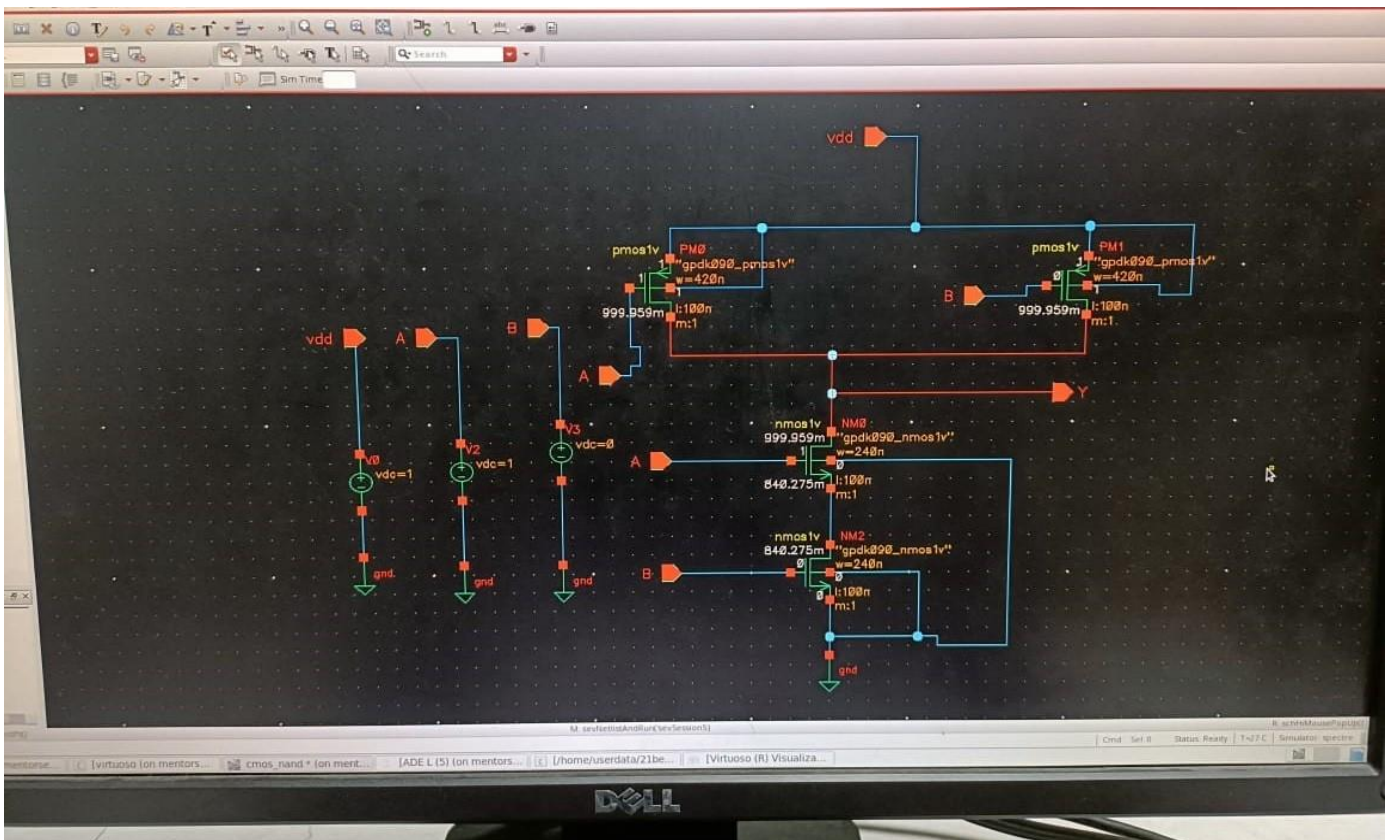

3 Transient Analysis:

 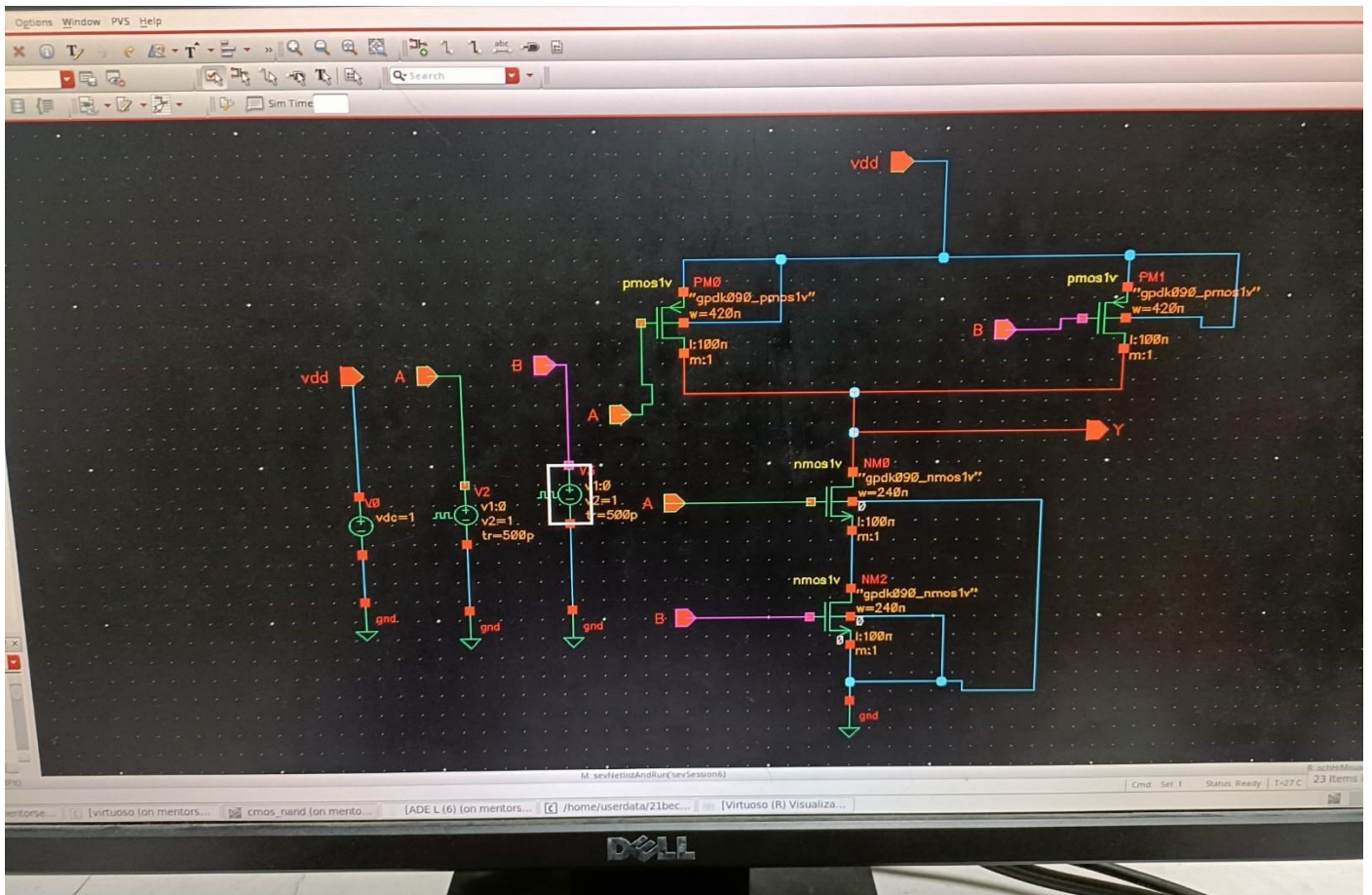

Inference: When either A or B is 1, the graph is similar to the CMOS Inverter DC Analysis graph but shifted towards the origin. For $A=B=0 \rightarrow 1$, it shows the same characteristics as CMOS Inverter DC Analysis graph but is away from the origin as due to different sizing ratio in CMOS inverter (3.5:1) and CMOS Nand Gate (3.5:2). When either A or B is 0, and the other is swept from 0 to 1, the output is approximately equal to 1 or VDD.

